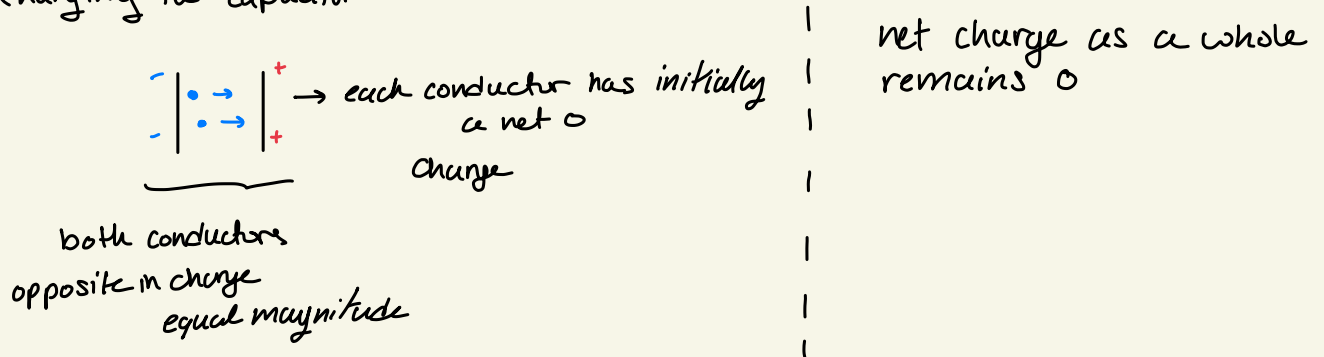



24.1 Capacitors and Capacitance

Any two conductors separated by an insulator form a capacitor.

Charging the capacitor



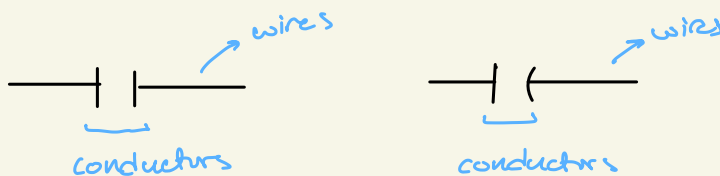In circuit diagrams a capacitor is represented by these symbols



- Capacitance of a capacitor $\rightarrow C = \frac{Q}{V_{ab}}$
 - Q \rightarrow magnitude of charge on each conductor
 - V_{ab} \rightarrow potential difference between conductors
- The larger the capacitance of a capacitor, greater the magnitude Q of charge on either conductor for a given potential difference and hence greater the amt of stored energy.

Capacitance only depends on the shapes and sizes, and position of conductors.



★ | let's say we wanted to store the same charge on a number of capacitors of different capacitance.

★ | The smaller the capacitance the larger potential difference we would need.

Important formulas in this section

Calculating Capacitance

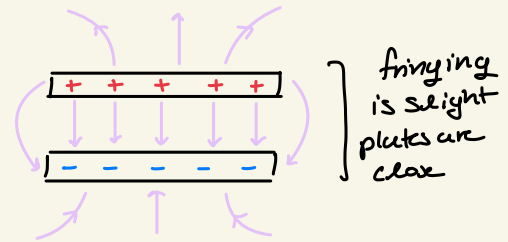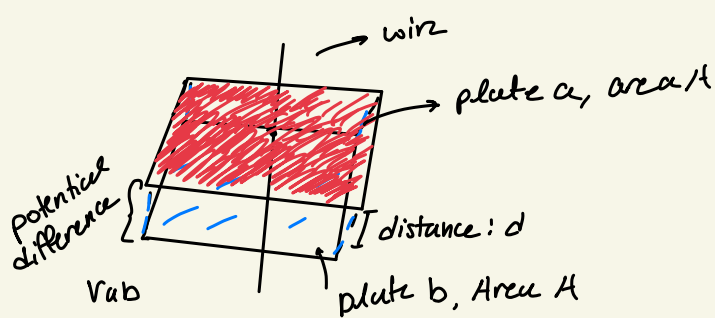- We can calculate capacitance C of a given capacitor by finding the potential difference V_{ab} between the conductors for a given magnitude of charge q



Finding electric field \vec{E} between the conductors is $\frac{\sigma}{2\epsilon_0} + \frac{\sigma}{2\epsilon_0}$

$$\vec{E} = \frac{\sigma}{\epsilon_0} ; \sigma \text{ magnitude of surface charge density (each plate)}$$

Since $\sigma = \frac{Q}{A}$ E can be expressed as:

$$\frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$

$$V_{ab} = \vec{E}d = \frac{Q}{\epsilon_0 A} \cdot d = \frac{1}{\epsilon_0} \cdot \frac{Qd}{A}$$

Thm.

$$C = \frac{Q}{V_{ab}} = \epsilon_0 \frac{A}{d}$$

← Capacitance of a parallel plate capacitor in vacuum
 ← mag of charge.
 ← area of each plate
 ← distance between plates
 ← Potential diff
 ← electric Constant

24.2 Capacitors in Series and Parallel

Capacitors are manufactured with certain standard capacitances and working voltages


Capacitors in series.

Two capacitors are connected in series by conducting wires between points a and b.

Initially uncharged when a potential difference is applied the capacitors become charged.

Capacitors in series:

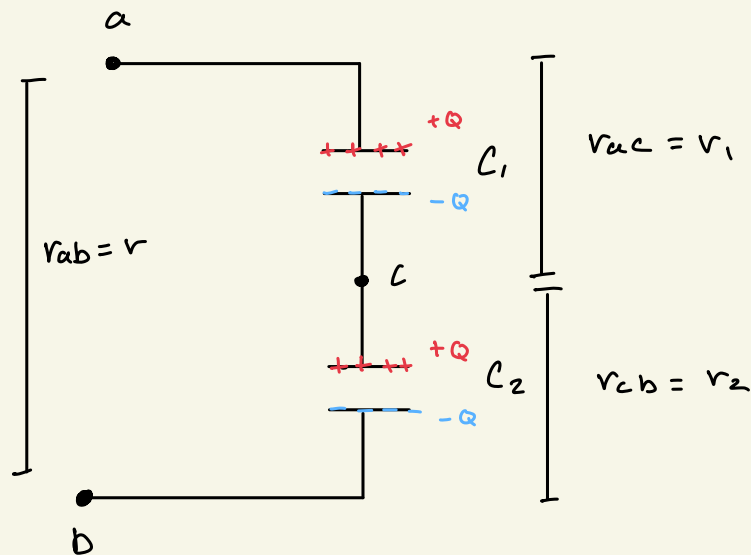- The capacitors have the same charge Q
- Their potential differences add : $V_{ac} + V_{cb} = V_{ab}$



Equivalent Capacitance is less than individual capacitances.

$$C_{eq} = \frac{Q}{V}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

Def. Capacitors in Series

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

↘ ↘ ↘
Capacitance of
individual
capacitors

Charge of the capacitors
are the same voltage is not


$$V = \frac{Q}{C}$$

$$V = Q \left(\frac{1}{C} + \frac{1}{C_n} \right)$$

Capacitors in parallel

- The capacitors have the same potential V
- The charge on each capacitor depends on its capacitance

$$Q_1 = C_1 V, \quad Q_2 = C_2 V$$

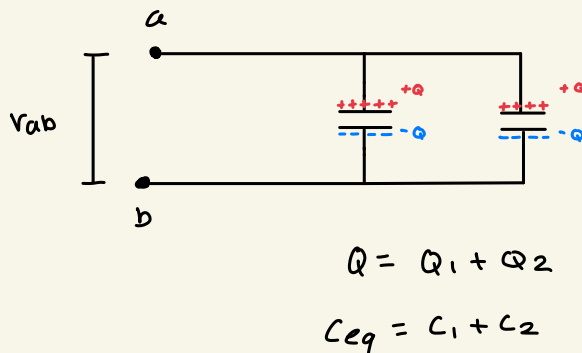


Voltage is the same in
parallel so,


$$\left. \begin{array}{l} Q_1 = C_1 V \\ Q_2 = C_2 V \end{array} \right\} \quad \underline{Q_1 + Q_2 = V(C_1 + C_2)}$$

Also important note Capacitance is in Farads.


Ex Problem:

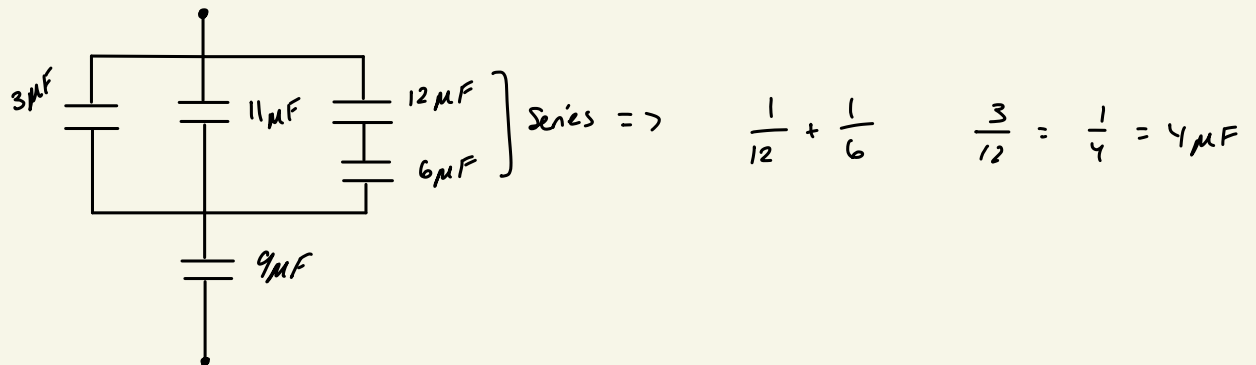

Step 2

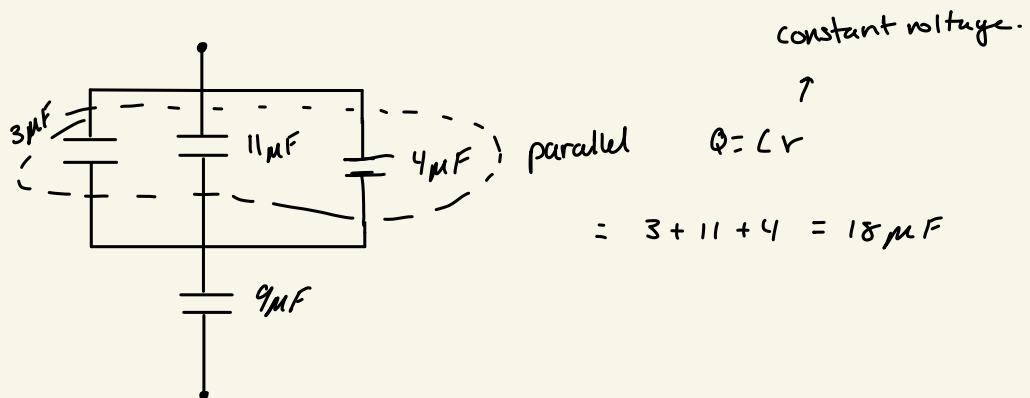

Step 3.1

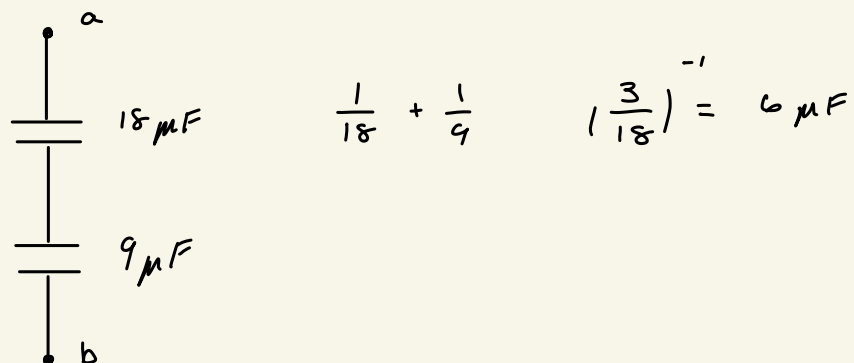

now we know capacitance if the potential diff $V_{ab} = 9.0V$, net charge is $Q = C_{eq} V_{ab} \Rightarrow Q = (6\mu F)(9.0V) = 54\mu C$